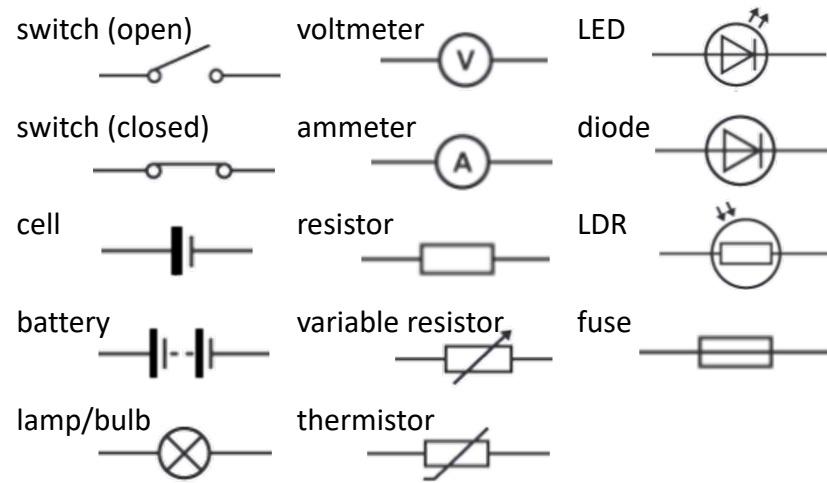


# Circuit Electricity 1

## 1. Circuit symbols

You must be able to remember the circuit symbols for these components, and use them when drawing a circuit:



**Remember:** when you draw a circuit diagram, the lines (wires) must be straight and the circuit must be complete!

## 3. Current

- Current is the **flow of electrical charge** around a circuit.
  - It's measured in **amps (A)** using an **ammeter connected in series with the component**.
  - A circuit must include a **source of potential difference** (a power source) in order for current to flow.
- We can calculate the charge flow using:


**Learn** (C) (A) (s)

$charge\ flow = current \times time$

You can use the equation triangle to re-arrange this:
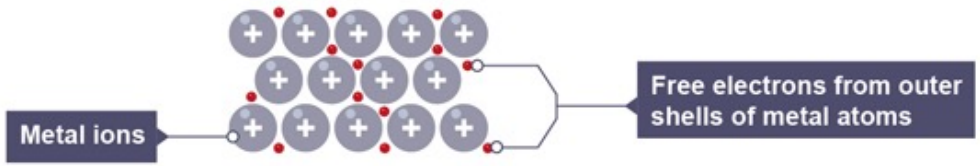
## 2. Charge

- Metals are conductors** of electricity
- Non-metals are insulators (poor conductors)
- This is due to their bonding: Metallic bonding creates a '**sea of delocalised electrons**' that can carry energy around a circuit.
- The unit of charge flow is the **coulomb (C)**. This represents a specific large number of electrons. 1 coulomb is equal to  $6 \times 10^{19}$  electrons.



## 4. Potential difference

- Potential difference (or voltage) is the driving force that **pushes** the charge around a circuit. It is the difference in energy between two points on a circuit.
  - Potential difference is the energy per unit of charge:
- $energy = charge\ flow \times potential\ difference$
- (J) **Learn** (C) (V)
- 
- It's measured in **volts (V)** using a **voltmeter connected in parallel over the component**.
  - Potential difference can be supplied using a **power source** (e.g. a battery)

## 5. Resistance

- Resistance is something that **slows down** the current.
  - It's measured in **ohms ( $\Omega$ )**.
  - The **bigger the resistance** of a component, the **less current gets through**.
- You can calculate the total resistance in a series circuit using:

total resistance

add together the individual resistances

**Learn**

$R_{total} = R_1 + R_2 + \dots$

- In parallel the total resistance of two resistors is less than the resistance of the smallest individual resistor.

# Circuit Electricity 2

## 6. Ohm's Law

The following equation is used to link potential difference, current and resistance:


$$\text{potential difference} = \text{current} \times \text{resistance}$$

(V)

(A)

(Ω)


Learn

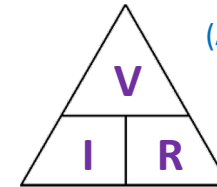

- The current through a circuit depends on the **potential difference** and **resistance**.
- If the potential difference is constant, then the **current will decrease** as **resistance is increased**.
- **Ohm's Law** states that current is **directly proportional** to potential difference for an ohmic conductor (if the temperature remains constant)
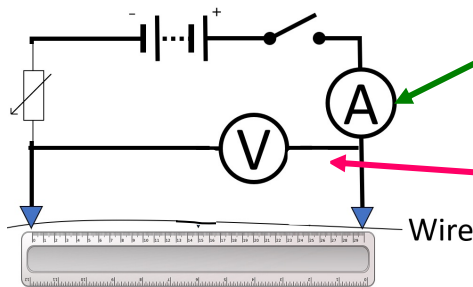
## 7. Required Practical: How does the length of a wire affect its resistance?

- You can calculate the resistance of a wire if you **measure the current and potential difference**.
- **Changing the length** of the wire and taking measurements will allow you to see if the resistance changes.



The **ammeter** measures the current through the circuit.

The **voltmeter** measures the potential difference across the wire.

Wire

As the current increases, the wire **heats up** which causes its resistance to **increase**. This reduces the **accuracy** of the experiment.


- You can increase the **accuracy** by:
  1. **stopping the current between readings** to let the wire cool
  2. using a **low current** to stop the wire heating up.
- You can increase the **precision** by using **pointed contacts** to connect to the wire so the uncertainty of the measurement is reduced.

## 8. Series and parallel circuits

There are two types of circuit: series and parallel.
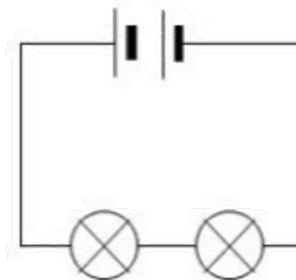
### Series Circuits


- All the components are connected in **one loop**.
- If one bulb breaks, the **whole circuit stops working**.
- The current is **the same everywhere**.
- The potential difference is **shared between components**.
- The total resistance is the **sum** of all the individual resistances.
- If you add more bulbs, they all **get dimmer**.



### Parallel Circuits

- The components are connected in **more than one loop**.
- If one bulb breaks, the **other branches will continue to work**.
- The current is **shared between each branch**.
- The potential difference is **the same across each component**.
- The total resistance is **less than** the smallest individual resistance.
- If you add more bulbs, they all **stay the same brightness**.

branches

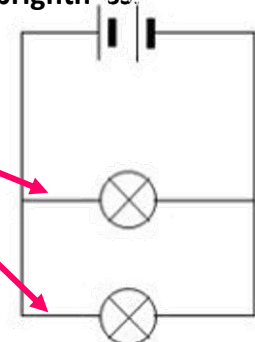

# Circuit electricity 3


## 9. Required Practical: I-V characteristics of different components

There are two types of conductor:

### Ohmic

- The resistance remains **constant** when you change the current
- The current is **directly proportional** to the potential difference
- If you drew a graph of I against V, it would be a **straight line through (0,0)**

Example: a resistor at constant temp.

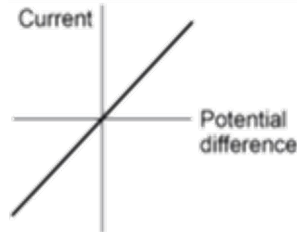


### Non-Ohmic

- The resistance **does** change with current


#### Example 1: a filament lamp

The resistance increases as it heats up

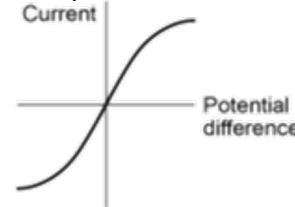

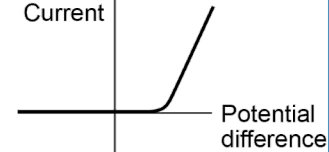
#### Example 2: a diode

Current can only flow in one direction, so resistance is very high the other way



## 10. Thermistors and LDRs

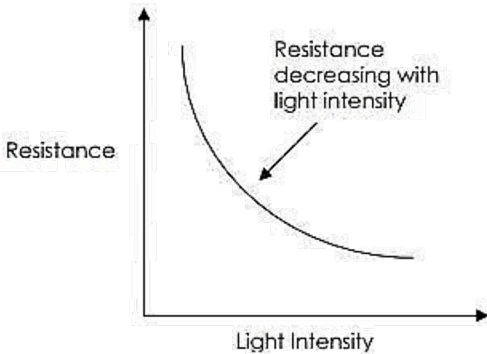

### Light Dependent Resistor (LDR)


The resistance **decreases** as the light gets **brighter**.

Example: **street lights** use these so they turn on when it gets dark
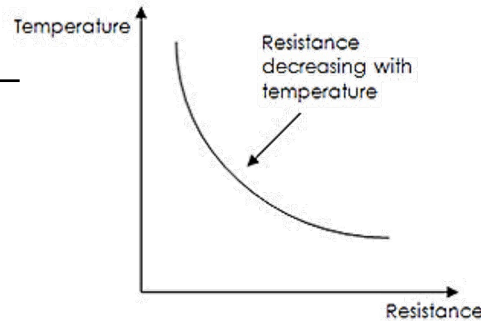
### Light Dependent Resistor

As light intensity increases the resistance decreases. They are **not** inversely proportional, it is an inverse square relationship.

$$\text{light intensity} = \frac{1}{\text{distance}^2}$$



### Thermistor

The resistance **decreases** as temperature **increases**.

Example: used in **thermostats** to turn on the heating when it gets cold

### Thermistor

Temperature is inversely proportional to resistance. This can be proved using the table of results. The product of the IV x DV will be the same for every row of data.

### Applications

As both an LDR and thermistor have low resistance at high temperature or light intensity, a parallel circuit is needed to use them to turn on lights or heaters.

